Shaka-Smooth ©Copyright 2001, Jay Doyle

Based upon original Shaka designs by Aron Nelson, Jack Orman, and Doug Hammond

Notes: - AI can be any op amp. Power connections and isolation of other op amp assumed.

- D1, D2, D3 are all 1N4148, but may be any type, adjust to taste.
- All Resistors 1/4 W, 5%.
- All Caps film types.
- All Pots linear.

Modifications:

- C2, C5, and C8 and all coupling capacitors; lower values roll of more bass.
- C4 Controls bass roll off of op amp gain stage, decrease value to roll of more bass.
 R6 has no series resistance to allow rolling the gain completely off to use the op amp stage as an input buffer. Adding series resistance will raise minimum gain.
- R7 can be bypassed by low value caps to preserve high frequencies at low drive settings.
- R9 controls gain of FET stage. Higher values lower gain.
- Sum of C9 and C10 determines high end roll off corner frequency of Tone control.
- More capacitance lowers roll off.
- Diode arrangement may be any conbination of diodes or diode connected transistors.
- Remove D2 for symmetrical clipping.

